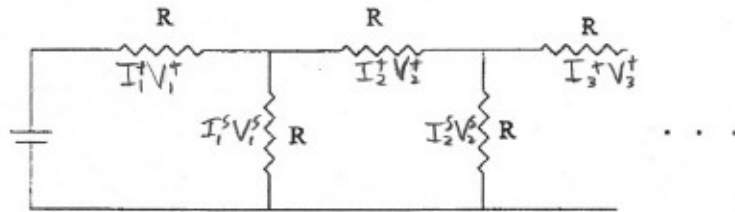
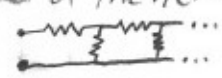


12. Electricity and Magnetism (Fall 2002)

A voltage is applied to the infinitely long resistor network shown below. Each resistor has the same resistance R . Calculate the power dissipated in each resistor.



First we find the total resistance of the network, \tilde{R} .
Let \tilde{R} be the resistance of 

$$\begin{aligned} \text{Then } \tilde{R} &= R + \frac{1}{\frac{1}{R} + \frac{1}{\tilde{R}}} \\ \Rightarrow \tilde{R} \left(\frac{1}{R} + \frac{1}{\tilde{R}} \right) &= R \left(\frac{1}{R} + \frac{1}{\tilde{R}} \right) + 1 \\ \Rightarrow \frac{\tilde{R}}{R} + 1 &= 1 + \frac{R}{\tilde{R}} + 1 \\ \Rightarrow \frac{\tilde{R}}{R} &= \frac{R}{\tilde{R}} + 1 \\ \Rightarrow \tilde{R}^2 &= R^2 + R\tilde{R} \\ \Rightarrow \tilde{R}^2 - R\tilde{R} - R^2 &= 0 \\ \Rightarrow \tilde{R} &= \frac{1}{2} [R \pm \sqrt{R^2 + 4R^2}] \\ \Rightarrow \tilde{R} &= \frac{1}{2} R (1 + \sqrt{5}) \quad \text{Since it must be pos.} \end{aligned}$$

Let V_n^+ , V_n^S be the voltage drop across the top, side resistors.

$$\text{By Ohm's Law, } I_n^+ = \frac{V_n^+}{R} = \frac{V_{n-1}^S}{\tilde{R}} \quad (1)$$

$$\text{By Kirchoff's Loop rule, } V_n^+ + V_n^S = V_{n-1}^S \quad (2)$$

$$(2) \rightarrow (1): \frac{V_{n-1}^S - V_n^S}{R} = \frac{V_{n-1}^S}{\tilde{R}}$$

$$\Rightarrow \frac{V_n^S}{R} = \frac{V_{n-1}^S}{R} - \frac{V_{n-1}^S}{\tilde{R}} = \left(\frac{1}{R} - \frac{1}{\tilde{R}} \right) V_{n-1}^S$$

$$\Rightarrow V_n^S = \left(1 - \frac{R}{\tilde{R}} \right) V_{n-1}^S$$

$$\Rightarrow V_n^S = \left(1 - \frac{R}{\tilde{R}} \right)^n V$$

$$\text{And by (1), } V_n^+ = \frac{R}{\tilde{R}} V_{n-1}^S = \frac{R}{\tilde{R}} \left(1 - \frac{R}{\tilde{R}} \right)^{n-1} V$$

$$\text{Therefore } P_n^S = \frac{(V_n^S)^2}{R} = \frac{V^2}{R} \left(1 - \frac{R}{\tilde{R}} \right)^{2n}$$

$$\text{and } P_n^+ = \frac{(V_n^+)^2}{R} = \frac{V^2 R}{\tilde{R}} \left(1 - \frac{R}{\tilde{R}} \right)^{2n-2}$$